

(FOR THE CANDIDATES ADMITTED

23UDA102

DURING THE ACADEMIC YEAR 2023 ONLY)

REG.NO. :

N.G.M. COLLEGE (AUTONOMOUS) : POLLACHI

END-OF-SEMESTER EXAMINATIONS: NOVEMBER 2023

BSC COMP.SCIENCE WITH DA(SF)

MAXIMUM MARKS: 75

SEMESTER:1

TIME: 3 HOURS

**PART - III**

**23UDA102 – DIGITAL ELECTRONICS**

**SECTION – A**

**(10 X 1 = 10 MARKS)**

**ANSWER THE FOLLOWING QUESTIONS.**

**(K1)**

1. Boolean Algebra is also called

- a) Switching algebra    b) Arithmetic algebra    c) Linear algebra    d) Algebra

2. The NAND gate is AND gate followed by .....

- a) NOT gate            b) OR gate            c) AND gate            d) None of the above

3. Which computer language that is written in binary codes only is \_\_\_\_\_

- a) machine language    b) C            c) C#            d) pascal

4. How many types of logic families exist?

- a) Two            b) Six            c) Four            d) Seven

5. When both inputs of a J-K flip-flop is low than cycle, the output will \_\_\_\_\_

- a) Be invalid            b) Change            c) Not change            d) Toggle

**ANSWER THE FOLLOWING IN ONE (OR) TWO SENTENCES**

**(K2)**

6. Mention the commonly used code for representing alphanumeric information?

7. Define combinational circuit

8. Define De Morgan's law.

9. What is demultiplexer?

10. Differentiate between latch and flip flop.

**SECTION – B**

**(5 X 5 = 25 MARKS)**

**ANSWER EITHER (a) OR (b) IN EACH OF THE FOLLOWING QUESTIONS.**

**(K3)**

11. a) Describe Hamming code

**(OR)**

b) Compute binary multiplication 11011.101 by 101.111

(CONT..2)

12.a) Sketch 2-input Exclusive NOR Gate

**(OR)**

b) Sketch the basic gates with its symbol truth table

13.a) Compute two variable and three variable K map

**(OR)**

b) Describe Boolean Functions and minterms and Maxterms.

14.a) Explain the functions of Multiplexers with Circuit.

**(OR)**

b) What conclusions can you draw for Encoders? Justify

15.a) Demonstrate the Rs flipflop with its truth table.

**(OR)**

b) Describe the logic Circuit of T flipflop with truth table.

### SECTION – C

**(5 X 8 = 40 MARKS)**

**ANSWER EITHER (a) OR (b) IN EACH OF THE FOLLOWING QUESTIONS. (K4 (Or) K5)**

16. a) Convert 5C6 (Hexadecimal) into binary decimal.

**(OR)**

b) Convert  $1073_{10}$  into a binary number

17. a) Applications of XOR Gate

**(OR)**

b) Explain NAND, NOR and XNOR get its truth table.

18. a) Evaluate De Morgan's Law statement and Proof with example.

**(OR)**

b) Examine the Boolean Algebra with example.

19.a) Construct the full adder and prepare its truth table

**(OR)**

b) Examine the working of master slave flipflop

20.a) Discuss the asynchronous counter with its timing diagram and truth table.

**(OR)**

b) Outline the triggering Flip Flop and Compare the Various flipflops.